

II B.Tech. I Semester Regular Examinations, November -2008
DIGITAL LOGIC DESIGN
 (Common to Computer Science & Engineering, Information Technology and
 Computer Science & Systems Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Convert the following number with indicated bases to decimal [4×2=8]
 - i. $(1\ 0\ 1\ 1\ 1\ 1)_2 =$
 - ii. $(A\ 3\ B)_{16} =$
 - iii. $(2\ 3\ 7)_8 =$
 - iv. $(4\ 3)_5 =$
- (b) Obtain the 1's and 2's complements of the following binary numbers [4×2=8]
 - i. $1\ 1\ 1\ 0\ 1\ 0\ 1\ 0 =$
 - ii. $0\ 1\ 1\ 1\ 1\ 1\ 1\ 0 =$
 - iii. $1\ 0\ 0\ 0\ 0\ 0\ 0\ 0 =$
 - iv. $0\ 0\ 0\ 0\ 0\ 0\ 0\ 0 =$
2. (a) Simplify the following Boolean expression to a minimum number of literals.
 - i. $F = (B\ \overline{C} + \overline{A}\ D) (A\ \overline{B} + C\ \overline{D})$
 - ii. $F = WYZ + XY + X\ \overline{Z} + YZ$
- (b) Express the following function in sum of minterms and product of maxterms.
 $F(A, B, C, D) = \overline{B}\ D + \overline{A}\ D + BD$ [8+8]
3. Implement the following Boolean function with NAND gates
 $F(x,y,z) = \Sigma (1,2,3,4,5,7)$. [16]
4. Design a code converter that converts BCD to excess - 3 code. [16]
5. (a) Discuss in detail about sequential circuit.
 (b) Construct a JK flip-flop using a D flip-flop, a 2-to-1 multiplexer and inverter. [8+8]
6. (a) Design a serial Adder in shift registers.
 (b) Write a HDL behavioral description of shift register. [8+8]
7. (a) Explain about internal construction of 4×4 RAM
 (b) Design a combinational circuit using a ROM. The circuit accepts a 3-bit number and generates an output binary number equal to the square of the input number. [8+8]
8. Explain about SR Latch with example. [16]

II B.Tech. I Semester Regular Examinations, November -2008
DIGITAL LOGIC DESIGN
 (Common to Computer Science & Engineering, Information Technology and
 Computer Science & Systems Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Convert the following numbers. [4×=8]
 - i. $(53)_{10} = ()_2$
 - ii. $(231)_4 = ()_{10}$
 - iii. $(1\ 1\ 0\ 1\ 1\ 0\ 1)_2 = ()_8$
 - iv. $(4D.56)_{16} = ()_2$
- (b) Add and subtract in binary [4×=8]
 - i. 1 1 1 1 and 1 0 1 0
 - ii. 1 1 0 1 1 0 and 1 1 1 0 1
 - iii. 1 0 0 1 0 0 and 1 0 1 1 0
 - iv. 1 1 0 1 0 0 1 and 1 1 0 1 1
2. (a) Implement the following Boolean function using AND, OR and inverter gates.
 $F = xy + \bar{x}\bar{y} + \bar{y}z$.
- (b) Using the rules of boolean algebra, simplify the expressions that follow to the fewest total number of literals. [8+8]
 - i. $f = A\bar{B} + ABC + A\bar{C}D$
 - ii. $f = B + AD + BC + [B + A(C + D)]^1$
3. Simplify the following Boolean function using four-variable map.
 $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15) + d(0, 2, 5)$. [16]
4. (a) Explain carry propagation in parallel adder with a neat diagram.
 (b) What is a decoder? Construct a 4×16 decoder with two 3×8 decoders. [8+8]
5. A Sequential circuit with two D flip-flops A and B, two inputs x and y and one output z is specified by the following next-state and output equation. [16]

$$A(t + 1) = \bar{x}y + xA$$

$$z = B$$

$$B(t + 1) = \bar{x}B + xA$$
 - (a) Draw the logic diagram of the circuit.
 - (b) List the state table for the sequential circuit.
 - (c) Draw the corresponding state diagram.
6. (a) Write about the HDL behavioral description of a 4-bit shift register.

- (b) Write about serial adder. [8+8]
7. Explain about error detection and correction with example. [16]
8. (a) Write a procedure for analysing an asynchronous sequential circuit with SR latch.
- (b) Explain in detail about debounce circuit. [8+8]

II B.Tech. I Semester Regular Examinations, November -2008
DIGITAL LOGIC DESIGN
 (Common to Computer Science & Engineering, Information Technology and
 Computer Science & Systems Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Perform the following binary multiplication operations
 - i. $100010 \times 001010 =$
 - ii. $001100 \times 011001 =$
 - iii. $000100 \times 010101 =$
 (b) Write the one's and two's complements of the following example.
 - i. 0011001
 - ii. 1110011
 - iii. 111111. [10+6]

2. (a) State and explain the Duality principle with example.
 (b) Given the Boolean function

$$F = x\bar{y}z + \bar{x}yz + \bar{w}xy + w\bar{x}y + wxy$$
 - i. Obtain the truth table of the function
 - ii. Draw the logic diagram using the original Boolean expression
 - iii. Simplify the function to a minimum number of literals using Boolean algebra. [6+10]

3. Find all the prime implicants for the following Boolean functions and determine which are essential.

$$F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$$
 [16]

4. (a) What is meant by encoder?
 (b) Design a 4 - input priority encoder. [4+12]

5. Write the HDL behavioural description of a
 - (a) D flip - flop
 - (b) F flip - flop. [8+8]

6. (a) Design a Serial Adder.
 (b) Write a HDL behavioural description of shift register. [8+8]

7. (a) Explain about internal construction of 4×4 RAM.

- (b) Design a combinational circuit using a ROM. The circuit accepts a 3-bit number and generates an output binary numbers equal to the square of the input number. [8+8]
8. (a) Explain the difference between asynchronous and synchronous sequential circuits.
- (b) Write about Hazards in sequential circuits. [8+8]

II B.Tech. I Semester Regular Examinations, November -2008
DIGITAL LOGIC DESIGN
 (Common to Computer Science & Engineering, Information Technology and
 Computer Science & Systems Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Find the decimal equivalent of the following two's complement numbers.
 - i. 11111
 - ii. 10001
 - iii. 01010
 - iv. 10011
 - v. 10101
- (b) Explain about error Detecting code with example. [10+6]
2. (a) Simplify each of the following expressions
 - i. $ABC\bar{D} + \bar{A}\bar{B}CD + C\bar{D}$
 - ii. $(A + \bar{B})(\bar{A} + \bar{B} + D)(\bar{B} + C + \bar{D})$
- (b) Explain about positive and Negative logic in binary signals. [8+8]
3. Obtain
 - (a) Sum of product and
 - (b) Product of sum expressions for the function given below
 $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$ [16]
4. (a) Implement a Boolean function
 $F(x, y, z) = \Sigma(2, 4, 6)$ with a Multiplexer.
 - (b) Explain about Tri - State gates in digital systems. [8+8]
5. Design a sequential circuit with two JK flip - flops A,B with one input X and one out put Y.
 $A(t + 1) = Ax + Bx$
 $B(t + 1) = \bar{A}x$
 $Y = A\bar{x} + B\bar{x}$. [16]
6. (a) Design a serial Adder using shift register.
 - (b) Write a HDL behavioral description of shift register. [8+8]
7. (a) Explain about internal construction of 4×4 RAM with neat diagram.
 - (b) Design a combinational circuit using a ROM. The circuit accepts a 3- bit number and generates an output binary number equal to the square of the input number. [8+8]

8. (a) Explain the difference between asynchronous and synchronous circuit.
- (b) Define fundamental - mode operation.
- (c) Explain the difference between stable and unstable states.
- (d) What is the difference between an internal state and a total state.[4+4+4+4]
