

I B.Tech Regular Examinations, May/June 2008

ELECTRICAL CIRCUITS ANALYSIS

(Common to Electrical & Electronic Engineering and Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Distinguish between passive and active elements with suitable examples.
- (b) Find the voltage and current source equivalent representation of the following network across AB, as shown in figure 1b. [6+10]

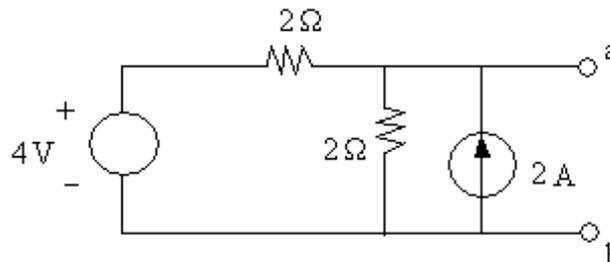


Figure 1b

2. (a) Derive an expression for the energy stored in an inductor and a capacitor.
- (b) Obtain an expression for Co-efficient of coupling. [10+6]
3. Obtain the rms value, average value, form factor and peak factor for a voltage of symmetrical square shape whose amplitude is 10V and time period is 40secs. [16]
4. (a) Three identical impedances of $(3+j4)\Omega$ are connected in delta. Find an equivalent star network such that the line current is the same when connected to the same supply.
- (b) Three impedances of $(7+j4)\Omega$, $(3+j2)\Omega$ and $(9+j2)\Omega$ are connected between neutral and the R, Y and B phases. The line voltage is 440V, Calculate.
 - i. The line currents and
 - ii. The current in the neutral wire.
 - iii. Find the power consumed in each phase and the total power drawn by the circuit. [4+12]
5. (a) Obtain the cut - set matrix for the network, as shown in figure 5a.

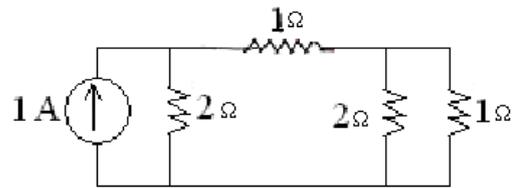


Figure 5a

- (b) For the network shown in figure 5b. Determine the power dissipated in 9Ω resistor using Mesh analysis. [6+10]

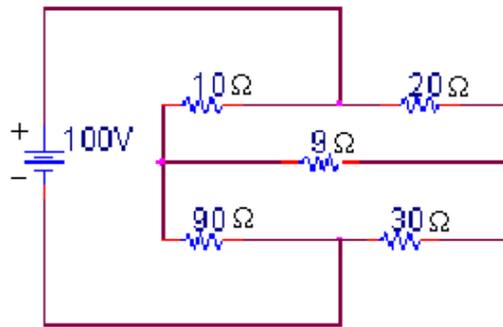


Figure 5b

6. (a) Using Norton's theorem, find the current through the load impedance Z_L as shown in figure 6a.

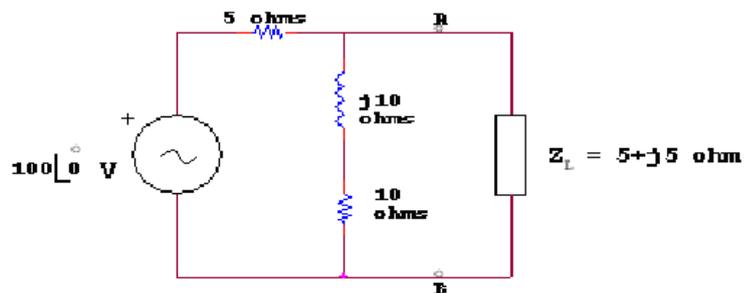


Figure 6a

- (b) State and explain reciprocity theorem. [10+6]
7. Derive an expression for the current response in R-L series circuit with a sinusoidal source. [16]
8. Find the Y - parameters for the bridged T-network as shown in figure 8. [16]

Code No: 07A1EC02

Set No. 1

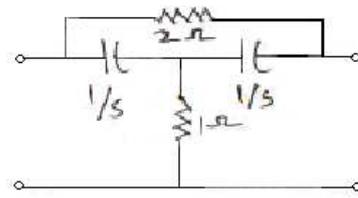


Figure 8

I B.Tech Regular Examinations, May/June 2008**ELECTRICAL CIRCUITS ANALYSIS****(Common to Electrical & Electronic Engineering and Instrumentation & Control Engineering)****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions
All Questions carry equal marks**

1. (a) A bridge network ABCD is arranged as follows:
Resistance between terminals AB, BC, CD, DA and BD are 10 ohms, 30 ohms, 15 ohms, 20 ohms and 40 ohms respectively. A 4V battery is connected with negligible internal resistance between terminals A and C. Determine the current through each element in the network using network reduction techniques.
- (b) Three equal resistances are available. Find
 - i. Two ratios of the equivalent resistances when they are connected in parallel.
 - ii. The ratio of the current through each element when they are connected in parallel. [10+6]
2. A non-magnetic ring having a mean diameter of 30cm and a cross-sectional area of 4cm^2 is uniformly wound with two coils A and B one over the other. A has 100 turns and B has 250 turns. Calculate the mutual inductance between the coils. Also, calculate the emf induced in B when a current of 6A in A is reversed in 0.02secs. Derive the formulae used. [16]
3. Define form factor and peak factor of an alternating quantity. Calculate the average and rms value, the form factor and peak factor of a periodic current having the following values for equal time intervals, changing suddenly from one value to next: 0,40,60,80,100,80,60,40,0,-40,-60,-80 A. [16]
4. (a) Three identical impedances of $(3+j4)\Omega$ are connected in delta. Find an equivalent star network such that the line current is the same when connected to the same supply.
- (b) Three impedances of $(7+j4)\Omega$, $(3+j2)\Omega$ and $(9+j2)\Omega$ are connected between neutral and the R, Y and B phases. The line voltage is 440V, Calculate.
 - i. The line currents and
 - ii. The current in the neutral wire.
 - iii. Find the power consumed in each phase and the total power drawn by the circuit. [4+12]
5. (a) For the network shown in figure 5a draw the oriented graph and frame the cut-set matrix.

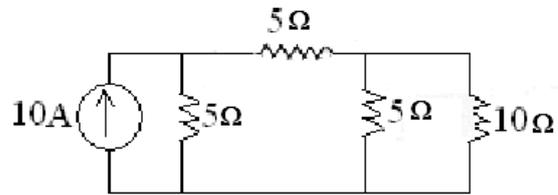


Figure 5a

- (b) Compute node voltages for the circuit as shown in figure 5b. [6+10]

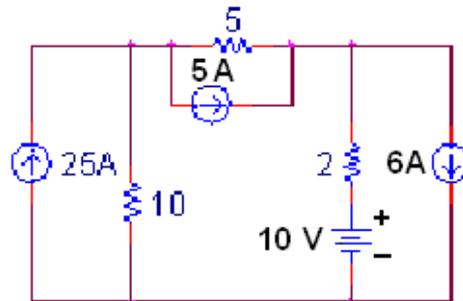


Figure 5b

6. (a) Find the value of R_L so that maximum power is delivered to the load resistance R_L as shown in figure 6a, and find the maximum power.

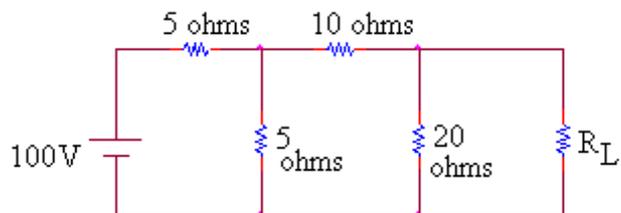


Figure 6a

- (b) State and explain Thevenin's theorem. [8+8]
7. Derive the expression for transient response of RLC series circuit with unit step input. [16]
8. Find the Z and transmission parameters for the resistance n/w shown in figure 8. [8+8]

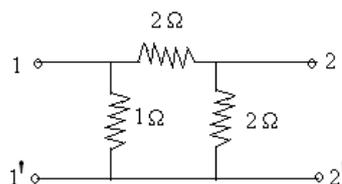


Figure 8

Code No: 07A1EC02

Set No. 2

I B.Tech Regular Examinations, May/Jun 2008

ELECTRICAL CIRCUITS ANALYSIS

(Common to Electrical & Electronic Engineering and Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Voltage of 60V d.c. is applied across two capacitors of $100 \mu\text{F}$. Find the voltage sharing between them if they are connected in series. What is the energy stored in each of the capacitors.
- (b) Find the equivalent capacitance between the terminals A and B in the circuit shown in figure 1b. [8+8]

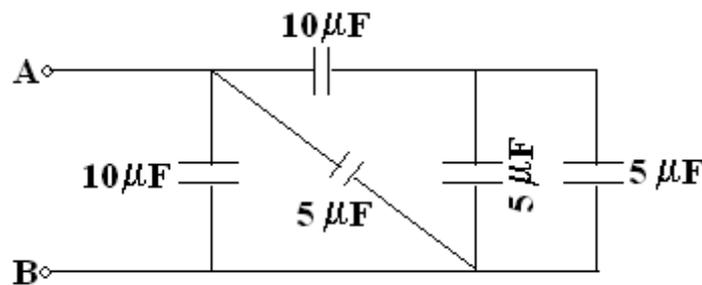


Figure 1b

2. The mean diameter of a steel ring is 40cm and flux density of $0.9 \text{ wb}/\text{m}^2$ is produced by 3500 ampere turns per metre. If the cross-section of the ring be 15 cm^2 and the number of turns 440, calculate
 - (a) The exciting current,
 - (b) The self inductance
 - (c) The exciting current and the inductance when an air gap of 2cm is cut in the ring, the flux density being the same. Ignore leakage and fringing. [16]
3. (a) Derive an expression for the current, impedance, average power for a series RC circuit excited by a sinusoidally alternating voltage and also find the power factor of the circuit. Draw the phasor diagram.
- (b) A series R-L series circuit having a resistance of 4Ω and 3 ohms inductive reactance is fed by 100V, 50Hz, 1- ϕ supply. Find current, power drawn by the circuit and power factor. [8+8]
4. (a) Explain how power is measured in three phase delta connected load using two wattmeters.
- (b) A balanced mesh connected load of $(8+j6)\Omega$ per phase is connected to a 3-phase, 50Hz, 230V supply. Calculate

- i. line current
- ii. Power factor
- iii. Reactive volt-ampere and
- iv. Total volt-ampere.

[8+8]

5. (a) For the network shown in figure 5a draw the oriented graph and frame the cut-set matrix.

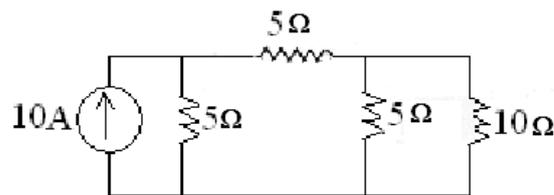


Figure 5a

(b) Compute node voltages for the circuit as shown in figure 5b. [6+10]

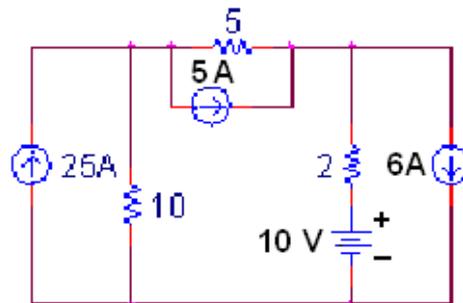


Figure 5b

6. (a) Find the current through the branch A-B of the network shown in the figure 6a using Thevenins theorem.

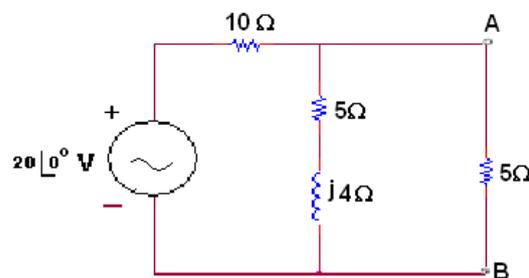


Figure 6a

(b) State and explain compensation theorem. [6+10]

7. Derive an expression for the current response in R-L series circuit with a sinusoidal source. [16]

8. Find the transformed Z - parameters of the n/w shown in figure 8: [16]

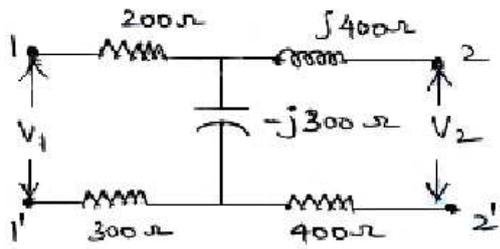


Figure 8

I B.Tech Regular Examinations, May/June 2008

ELECTRICAL CIRCUITS ANALYSIS

(Common to Electrical & Electronic Engineering and Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

- Two resistances when they are in series has an equivalent resistance of 9 ohms and when connected in parallel has an equivalent resistance of 2 ohms. Find the resistances and the ratio of the voltage and current sharing between these elements if supply voltage is 50V.
 - Find the equivalent resistance between the terminals AB in the network as shown in figure 5b, if each has a resistance of R ohms and hence find the total current, current through each of the element if the total voltage is 45V. [8+8]

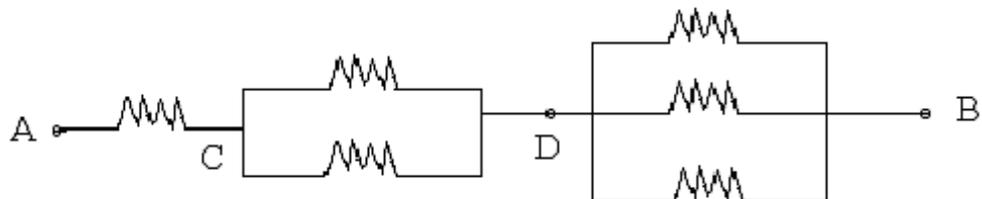


Figure 5b

- The number of turns in a coil is 250. When a current of 2A flows in the coil, the flux in the coil is 0.3mwb. When the current is reduced to zero in 2ms, the voltage induced in a coil lying in the vicinity of the coil is 63.75V. If the co-efficient of coupling between the coils is 0.75, find.

 - The self inductance of two coils.
 - Mutual inductance.
 - Number of turns in the second coil.

Derive the formulae used. [16]
- Why the rms values of an alternating quantity is more important than its average value. Find the rms value of the resultant current in a conductor which carries simultaneously sinusoidal alternating current with a maximum value of 15A and direct current of 15A, by deriving necessary expressions. [16]
- A symmetrical 3-phase, 3-wire, 440V supply is connected to a star connected load. The impedances in each branch are : $Z_1=(2+j3)\Omega$, $Z_2=(1-j2)\Omega$, $Z_3=(3+j4)\Omega$. Find its equivalent delta connected load. Hence find the phase and line currents and the total power consumed in the circuits. [16]
- Write the tie - set schedule for the network shown in figure 5a

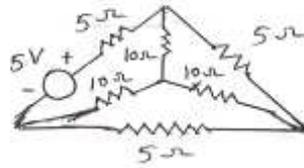


Figure 5a

- (b) Using mesh analysis, determine the voltage V which gives a voltage of $50V$ across $10\ \Omega$ resistor shown in figure 5b. [6+10]

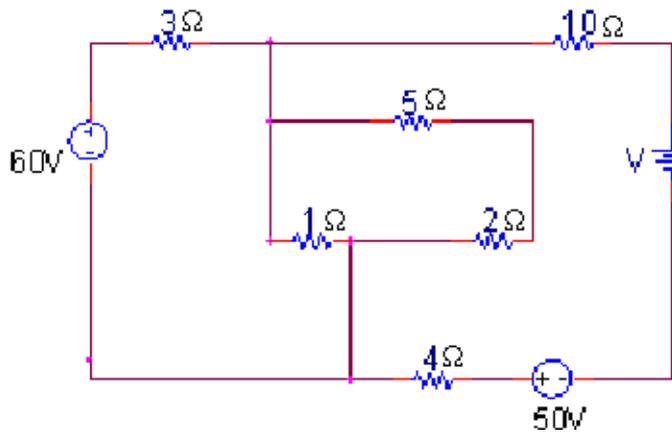


Figure 5b

6. (a) Obtain Norton's equivalent across terminals A and B for network shown in figure 6a.

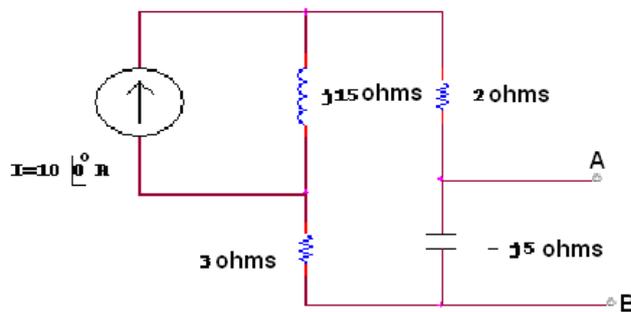


Figure 6a

- (b) State and explain Maximum power transfer theorem. [10+6]
7. In the circuit shown in the figure 7, the switch is put in position - 1 for 1 m sec and then thrown to position - 2. Find the transient current in both intervals. [16]

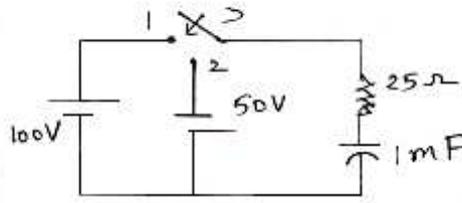


Figure 7

8. (a) Find the Y parameters of the pie shown in figure 8a:

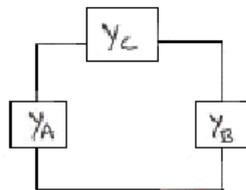


Figure 8a

(b) Find the Z parameters of the T- network shown in figure 8b. Verify the network is reciprocal or not. [4+12]

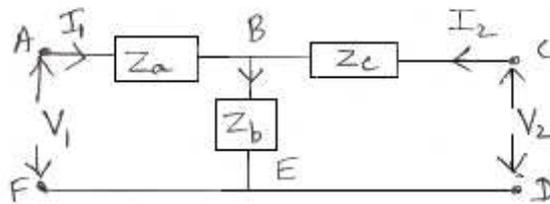


Figure 8b
