

Code No: 52202/MT

M.Tech. – II Semester Regular Examinations, September, 2008

HVDC TRANSMISSION
**(Common to Power Electronics & Electric Drives/
Electrical Power Systems/ Power & Industrial Drives)**

Time: 3 hours

Max. Marks:60

Answer any FIVE questions
All questions carry equal marks

- - -

- 1.a) With the help of a schematic diagram discuss about the major components of a HVDC converter station.
b) Explain the power handling capabilities of HVDC lines.
- 2.a) Derive the expression for DC voltage of a six pulse bridge converter, considering gate control and source reactance.
b) Obtain the equivalent circuit for rectifier operation of a Graetz circuit.
- 3.a) Discuss about various types of AC filters that can be used for harmonic reduction.
b) Calculate AC harmonics of a 12-pulse converter using fourier analysis. Neglect overlap and assume that direct current is ripple free?
- 4.a) Draw converter controller characteristic and explain why it is desirable to have current control at rectifier station and CEA control at inverter station.
b) Explain pulse frequency control firing scheme.
- 5.a) Discuss harmonic instability problems in HVDC systems.
b) What is meant by reactive power control? How it is achieved? Explain in detail.
- 6.a) Discuss the advantages and disadvantages of series and parallel MTDC systems.
b) Explain Two ACR method for control of MTDC systems.
- 7.a) Discuss about various faults that can occur in converts.
b) Explain the over voltage protection in converter station.
8. Write short notes on the following:
 - (i) DC line protection
 - (ii) Corona effect on DC lines
 - (iii) DC breakers.

* * * * *