

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
II.B.TECH - I SEMESTER REGULAR EXAMINATIONS NOVEMBER, 2009
DIGITAL LOGIC DESIGN
(Common to CSE, IT, CSS)

Time: 3hours

Max.Marks:80

Answer any FIVE questions
All questions carry equal marks

- - -

1. a) Express the Excess-3 code as a Gray code
b) What is meant by Self complementing codes? Give an example and explain.
c) What are the properties of Boolean algebra? [8+8]
2. a) State and prove De'Morgan's theorems
b) Prove that NAND and NOR gates are universal gates
c) Design a 2 input XOR and XNOR using NAND and NOR gates respectively by using only 4 gates each. [16]
3. a) Design a FULL adder / subtractor unit using only NAND gates
b) Minimize the given function $f = \sum(1, 2, 3, 5, 7, 9, 11, 13)$ use K map method. [8+8]
4. a) Design a Priority encoder of 4 bit.
b) Write HDL code to model the above encoder. [8+8]
5. a) Design a finite state machine which can detect the sequence 0010 by using JK flip flops. [8+8]
b) Write HDL program in Behavioral model to design the above sequence detectors.
6. a) Design an asynchronous modulo-6 counter. Use SR flip flop in the design.
b) Write HDL program to model in structural model. [8+8]
7. a) Design a 4 bit number square generated using ROM.
b) Write a brief note on sequential programmable devices. [8+8]
8. Write brief note on
a) Static and dynamic hazards.
b) Flow table generation in asynchronous limits in pulse mode. [8+8]
