

Code No: A5706
JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
M.Tech I Semester Examinations, October/November-2011
CPLD AND FPGA ARCHITECTURE AND APPLICATIONS
(VLSI SYSTEM DESIGN)

Time: 3hours

Max. Marks: 60

Answer any five questions
All questions carry equal marks

- - -

- 1.a) Explain about the ALTERA's third generation architecture of MAX7000 family with a neat diagram.
b) Compare the following programmable logic families of ROM, PLA and PAL. [12]
- 2.a) Explain about Lattice PLSI architecture.
b) Distinguish between FPGA and CPLD. [12]
- 3.a) Explain how ACTEL ACT2 FPGA family is architecturally close to MPGA. Compare RAM and anti fuse based FPGAS.
b) What are optimized reconfigurable cell arrays? Explain their features and performance. [12]
- 4.a) Explain about one hot state machine with state table and state diagrams.
b) Explain the advantages of one hot encoding with suitable examples. [12]
- 5.a) Explain the truth table and state diagram type design entry methods of FPGA Advantage Tool.
b) Explain the FPGA design flow of parallel controller as a case study. [12]
6. Design an 8-bit counter using D flip-flops. Write code for mentor graphic EDA Tool "FPGA Advantage" for this design. [12]
7. Design a digital system which performs a binary multiplication using ASM chart and design the controller of the system. Implement the same using PLA. [12]
8. Write short notes on
 - a) Meta stability and synchronization.
 - b) Non-register PLD architectures. [12]

* * * * *